_____ gate
Logic Diagram Symbol

_____ gate
Logic Diagram Symbol

Truth Table

A	B	X

Truth Table

A	B	X

Boolean Expression:

Boolean Expression:

_____ gate
Logic Diagram Symbol

Truth Table

A	X

Boolean Expression: